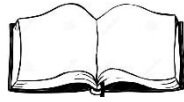


## Seminar 8: Lectures 15-16


**Print and answer** all questions found below.

**Please bring your completed worksheet to the Seminar Class.**<sup>1</sup>



## Question 1

- Define electromotive force (*emf*) and terminal voltage in a circuit.
- Calculate the terminal voltage across a battery with an (*emf*) of 12 V and internal resistance of  $0.5\ \Omega$ , when connected to a load resistor of  $11.5\ \Omega$ .
- Discuss the factors that influence terminal voltage in practical circuits.

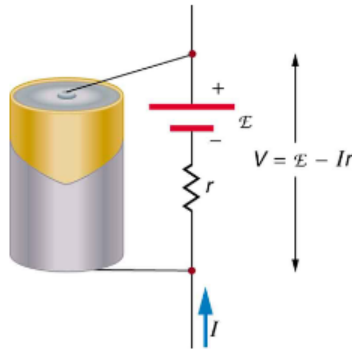[illegible]

<sup>1</sup> It is assumed that you have access to the standard physical constants.

## Seminar 8: Lectures 15-16

## Question 2

A car battery with a 12 V emf and an internal resistance of  $0.050\Omega$  is being charged with a current of 60 A. Note that in this process the battery is being charged.

- What is the potential difference across its terminals?
- At what rate is thermal energy being dissipated in the battery?
- At what rate is electric energy being converted to chemical energy?

[illegible]

## Seminar 8: Lectures 15-16

### Question 3

Three resistors having resistances of  $1.6\ \Omega$ ,  $2.4\ \Omega$  and  $4.8\ \Omega$

respectively, are connected in parallel to a 28.0 V battery that has negligible internal resistance. Find:


- the equivalent resistance of the combination,
- the current in each resistor,
- the total current through the battery,
- the voltage across each resistor, and
- the power dissipated in each resistor.
- Which resistor dissipates the most power, the one with the greatest resistance or the one with the least resistance? Explain why.

[illegible]

## Seminar 8: Lectures 15-16

### Question 4


- What is Kirchhoff's 1st and 2nd law?
- Find the currents flowing in the circuit provided using Kirchhoff's Rules.

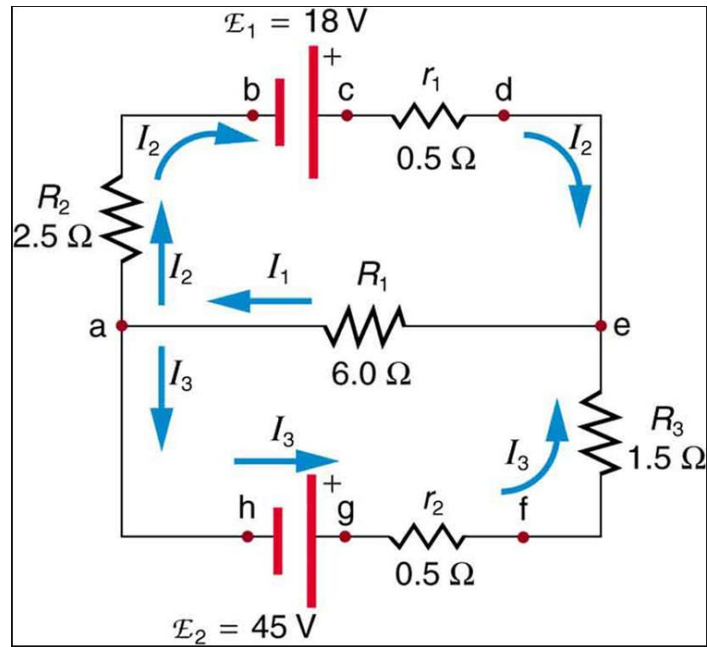This image shows a full page of white paper with horizontal dotted lines. The lines are evenly spaced and run across the width of the page, providing a guide for handwriting practice. There are no margins, text, or other markings on the page.

## Seminar 8: Lectures 15-16

### Question 5

Using the exact exponential treatment, determine how much time is required to charge an initially uncharged 100 nF capacitor through a 75.0 M $\Omega$  resistor to 90.0% of its final voltage in a RC circuit.

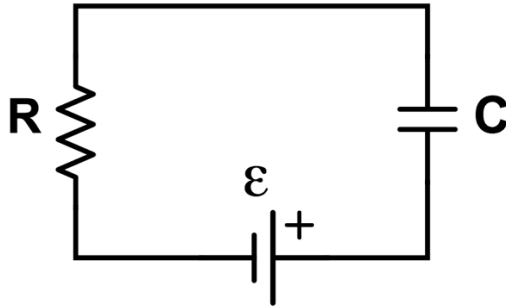[illegible]

### Question 6

- (a) What voltage will accelerate electrons to a speed of  $6 \times 10^7 \text{ m/s}$ ?
- (b) Find the radius of curvature of the path of a proton accelerated through this potential in a  $0.5 \text{ T}$  field and compare this with the radius of curvature of an electron accelerated through the same potential.

[illegible]

## Seminar 8: Lectures 15-16

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

### Question 7

An electron moving at  $4 \times 10^3 \text{ m/s}$  in a  $1.25 \text{ T}$  magnetic field experiences a magnetic force of  $1.4 \times 10^{-16} \text{ N}$ . What angle does the velocity of the electron make with the magnetic field? There are two answers.

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

## Seminar 8: Lectures 15-16

### Question 8

Consider a capacitor  $C$  being discharged through a resistor  $R$  as shown in the figure. The initial potential difference across the capacitor is  $3.0\text{ V}$ , the capacitance is  $2.70 \times 10^{-6}\text{ F}$ , and the resistance is  $1.80\ \Omega$ .

- (a) How long does it take for the charge on the capacitor to drop to one-fourth of its initial value?
- (b) Compute the initial charge and time constant.
- (c) How long does it take to discharge all but the last quantum of charge,  $1.60 \times 10^{-19}\text{ C}$ , if the initial potential difference across the capacitor is  $12.0\text{ V}$ , the capacitance is equal to  $3.50 \times 10^{-6}\text{ F}$ , and the resistance is  $2.0\ \Omega$ .

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

## Seminar 8: Lectures 15-16

## Extension Questions

### Question 9

A child's electronic toy is supplied by three 1.58 V alkaline cells having internal resistances of  $0.0200\Omega$  in series with a 1.53 V carbon-zinc dry cell having a  $0.100\Omega$  internal resistance. The load resistance is  $10.0\Omega$ .

- Draw a circuit diagram of the toy and its batteries.
- What current flows?
- How much power is supplied to the load?
- What is the internal resistance of the dry cell if it goes bad, resulting in only 0.500 W being supplied to the load?

[illegible]




## Seminar 8: Lectures 15-16

### Question 10

A network of five equal resistors  $R$  is connected to a battery  $\mathcal{E}$  as shown in the figure.

- Determine the current  $I$  that flows out of the battery.
- Use the value determined for  $I$  to find the single resistor  $R_{eq}$  that is equivalent to the five-resistor network.

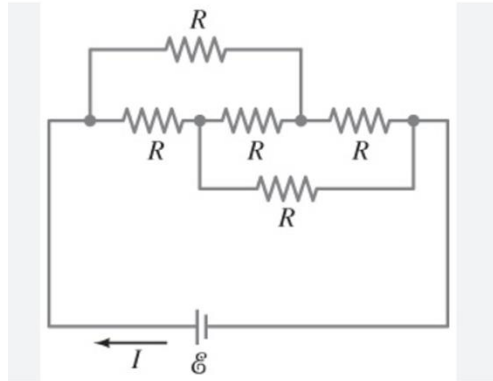[illegible]